

ANKARA YILDIRIM BEYAZIT UNIVERSITY

CENG205- Electrical Circuit and Electronic Devices

Homework 2

- (40p) The circuit shown in Figure-1 has been operating for along time when the switch is positioned at "a". It is moved to position "b" at $t=0$.
 - Obtain expressions for $i(t)$ and $V_C(t)$ valid for all values of t .
 - Determine the energy remaining in the capacitor at $t = 33 \mu\text{s}$.

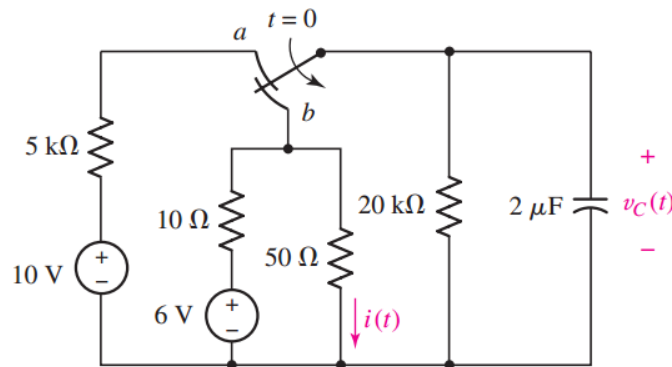


Figure 1 RC circuit analysis with natural and forced response

- (40p) For the two-source circuit of Fig. 2, note that one source is always on.
 - Obtain an expression for $i(t)$ valid for all t .


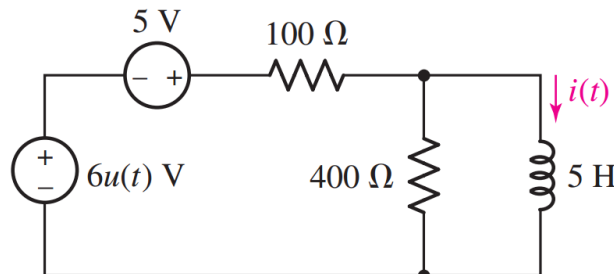


Figure 2 RL circuit analysis with natural and forced response

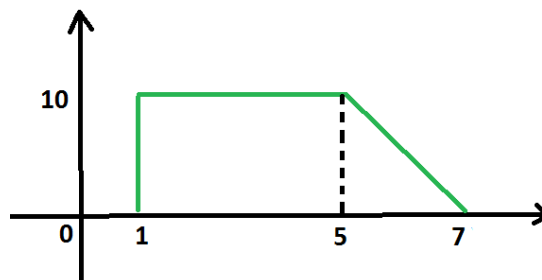- (20p) Find the representation of the following signal in terms of singularity functions (unit step, ramp and impulse function).



Dead-line: December 14, 2017 at 13:00.

Late submissions will be graded as -50 point for each day. Please do not copy the homework from any of your friend. Such plagiarism tendency will be punished as -50 from this homework.

GOOD LUCK!